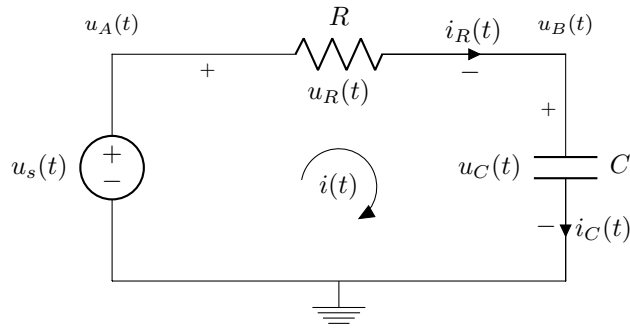


# RC Circuit Transient Analysis using Laplace Transform for both DC and AC Voltage Source

Aimilios's Circuits

September 29, 2018

## 1 RC Circuit



### 1.1 V-I Relations

$$u_R(t) = R \cdot i_R(t)$$

$$i_R(t) = \frac{1}{R} \cdot u_R(t)$$

$$u_C(t) = \frac{1}{C} \cdot \int_0^t i_C(t) dt + u_C(0)$$

$$i_C(t) = C \cdot \frac{du_C(t)}{dt}$$

### 1.2 V-I Relations to Mesh Current and Nodal Voltage


$$u_R(t) = u_A(t) - u_B(t)$$

$$i_R(t) = i(t)$$

$$u_C(t) = u_B(t)$$

$$i_C(t) = i(t)$$

## 2 Initial Conditions

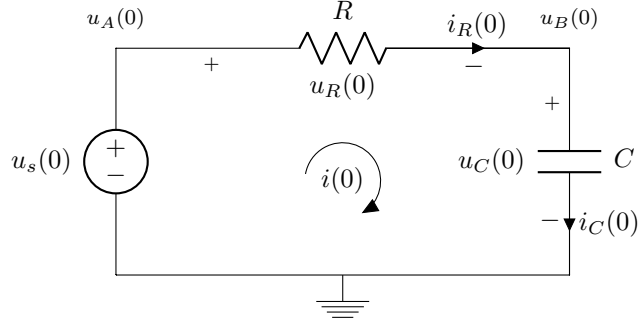

For  $t = 0$ :

Initial Capacitor Voltage:  $u_c(0)$ , so from the circuit:

$$\begin{aligned} u_B(0) - 0 &= u_c(0) \\ u_B(0) &= u_c(0) \end{aligned} \tag{1}$$

Kirchoffs Current Law in node A:

$$\begin{aligned} u_s(0) &= u_A(0) - 0 \\ u_A(0) &= u_s(0) \end{aligned} \tag{2}$$

Kirchoffs Current Law in node B:

$$\begin{aligned} i_R(0) &= i_C(0) \\ \frac{u_A(0) - u_B(0)}{R} &= C \frac{du_B(t)}{dt} \Big|_{t=0} \\ u'_B(0) &= \frac{1}{RC} (u_A(0) - u_B(0)) \\ u'_B(0) &= \frac{1}{RC} (u_s(0) - u_c(0)) \end{aligned} \tag{3}$$

Kirchoffs Voltage Law in loop:

$$\begin{aligned} -u_s(0) + u_R(0) + u_C(0) &= 0 \\ -u_s(0) + R * i_R(0) + u_C(0) &= 0 \\ -u_s(0) + R * i(0) + u_C(0) &= 0 \\ i(0) &= \frac{u_s(0) - u_C(0)}{R} \end{aligned} \tag{4}$$

All initial Conditions:

$$\begin{aligned}
u_A(0) &= u_s(0) \\
u_B(0) &= u_c(0) \\
u'_B(0) &= \frac{1}{RC}(u_s(0) - u_c(0)) \\
i(0) &= \frac{u_s(0) - u_c(0)}{R}
\end{aligned}$$

### 3 Mesh Analysis

#### 3.1 I Formula

$$\begin{aligned}
-u_s(t) + u_R(t) + u_C(t) &= 0 \\
-u_s(t) + R \cdot i_R(t) + \frac{1}{C} \cdot \int_0^t i_C(t) dt + u_C(0) &= 0 \\
-u_s(t) + R \cdot i(t) + \frac{1}{C} \cdot \int_0^t i(t) dt + u_C(0) &= 0 \\
\text{Laplace Transform: } -V_s(s) + R \cdot I(s) + \frac{1}{C} \frac{I(s)}{s} + \frac{u_C(0)}{s} &= 0 \\
I(s)(s + \frac{1}{RC}) &= \frac{1}{R}(sV_s(s) - u_C(0)) \\
I(s) &= \frac{1}{R}(sV_s(s) - u_C(0)) \frac{1}{(s + \frac{1}{RC})}
\end{aligned}$$

#### 3.2 Solution According to Source Voltage Signal

##### 3.2.1 For DC Signal

$$\begin{aligned}
u_s(t) &= U_s \cdot u(t) \\
V_s(s) &= \mathcal{L}\{u_s(t)\} = \frac{U_s}{s} \\
I(s) &= \frac{1}{R}(U_s - u_C(0)) \frac{1}{(s + \frac{1}{RC})}
\end{aligned}$$

##### 3.2.2 For AC Cosine Signal

$$\begin{aligned}
u_s(t) &= U_s \cdot \cos(\omega t) \\
V_s(s) &= \mathcal{L}\{u_s(t)\} = U_s \frac{s}{s^2 + \omega^2} \\
I(s) &= \frac{1}{R}(U_s \frac{s^2}{s^2 + \omega^2} - u_C(0)) \frac{1}{(s + \frac{1}{RC})}
\end{aligned}$$

### 3.3 Solution

#### 3.3.1 DC Solution

$$i(t) = \frac{Us - u_C(0)}{R} e^{(\frac{-t}{RC})}$$

#### 3.3.2 AC Cosine Solution

$$i(t) = \frac{Us \cdot C \cdot \omega \cdot \sin(\omega t) - Us \cdot C^2 \cdot R \cdot \omega^2 \cdot \cos(\omega t)}{R^2 \cdot C^2 \cdot \omega^2 + 1} - e^{(\frac{-t}{RC})} \cdot \frac{u_C(0) \cdot R^2 \cdot C^2 \cdot \omega^2 - Us + u_C(0)}{R \cdot (R^2 \cdot C^2 \cdot \omega^2 + 1)}$$

## 4 Nodal Analysis

### 4.1 V Formula

Kirchoffs Current Law in node A:

$$\begin{aligned} u_s(t) &= u_A(t) - 0 \\ u_A(t) &= u_s(t) \end{aligned} \tag{5}$$

Kirchoffs Current Law in node B:

$$\begin{aligned} i_R(t) &= i_C(t) \\ \frac{u_A(t) - u_B(t)}{R} &= C \frac{du_B(t)}{dt} \\ \frac{1}{RC} \cdot (u_A(t) - u_B(t)) - u'_B(t) &= 0 \\ \text{Laplace Transform: } \frac{1}{RC} \cdot V_A(s) - \frac{1}{RC} \cdot V_B(s) - (s \cdot V_B(s) - u_B(0)) &= 0 \\ \frac{1}{RC} \cdot V_A(s) - \frac{1}{RC} \cdot V_B(s) - s \cdot V_B(s) + u_B(0) &= 0 \\ \text{From (1),(5): } \frac{1}{RC} \cdot V_s(s) - \frac{1}{RC} \cdot V_B(s) - s \cdot V_B(s) + u_C(0) &= 0 \\ V_B(s) \cdot (s + \frac{1}{RC}) &= \frac{1}{RC} \cdot V_s(s) + u_C(0) \\ V_B(s) &= \frac{1}{RC} \cdot (V_s(s) + u_C(0)) \cdot \frac{1}{(s + \frac{1}{RC})} \end{aligned}$$

## 4.2 Solution According to Source Voltage Signal

### 4.2.1 For DC Signal

$$\begin{aligned}u_s(t) &= U s \cdot u(t) \\V_s(s) &= \mathcal{L}\{u_s(t)\} = \frac{U s}{s} \\V_B(s) &= \frac{1}{RC} \cdot (U s + u_C(0)) \cdot \frac{1}{(s + \frac{1}{RC})}\end{aligned}$$

### 4.2.2 For AC Cosine Signal

$$\begin{aligned}u_s(t) &= U s \cdot \cos(\omega t) \\V_s(s) &= \mathcal{L}\{u_s(t)\} = U s \frac{s}{s^2 + \omega^2} \\V_B(s) &= \frac{1}{RC} \cdot (U s \frac{s^2}{s^2 + \omega^2} + u_C(0)) \cdot \frac{1}{(s + \frac{1}{RC})}\end{aligned}$$

## 4.3 Solution

### 4.3.1 DC Solution

$$u_B(t) = U s + (u_C(0) - U s) \cdot e^{\left(\frac{-t}{RC}\right)}$$

### 4.3.2 AC Cosine Solution

$$U_B(t) = \frac{U s \cdot \cos(\omega t) + U s \cdot C \cdot R \cdot \sin(\omega t)}{R^2 \cdot C^2 \cdot \omega^2 + 1} + e^{\left(\frac{-t}{RC}\right)} \cdot \frac{u_C(0) \cdot R^2 \cdot C^2 \cdot \omega^2 + u_C(0) - U s}{R^2 \cdot C^2 \cdot \omega^2 + 1}$$